

## Electronics HW Problem Set

1. Using the basics of how a voltage divider circuit works, compute the voltage output, current draw from the 9V battery and the power dissipated in a load resistor in these two circuits:

Circuit 1:  $R_1 = 10\text{k}\Omega$  and  $R_2 = 10\text{k}\Omega$

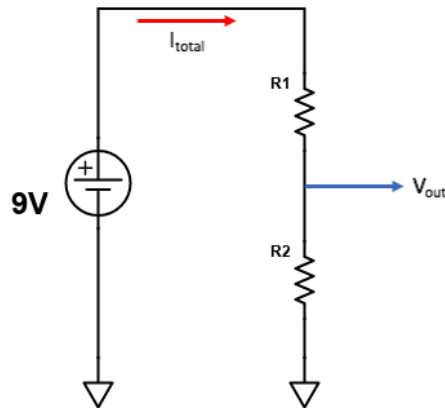


Figure 1a

Compute  $V_{\text{out}}$  (the output/measured voltage) and  $I_{\text{total}}$  for the circuit shown in Fig 1a.

Circuit 2:  $R_1 = 10\text{k}\Omega$ ,  $R_2 = 10\text{k}\Omega$  and  $R_3 = 5\text{k}\Omega$

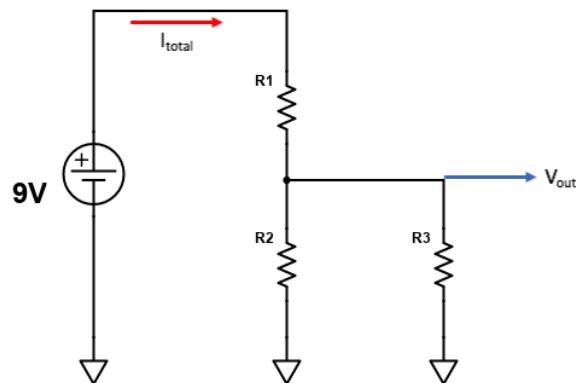


Figure 1b

Compute  $V_{\text{out}}$  and  $I_{\text{total}}$  for the circuit shown in Fig 1b. Using these results, compute the dissipated power in load resistor  $R_3$ .

2. Show that it is not possible to exceed the power rating of a  $\frac{1}{4}$  watt resistor of resistance greater than  $1\text{k}\Omega$ , no matter how you connect it, in a circuit operating from a 15 volt battery. (*Hint: think of at least two arrangements that could cause the maximum current to flow through the resistor*)
3. A current varies a function of time as shown in Figure 2. Predict and plot the voltage produced by this current flowing in an uncharged  $1\mu\text{F}$  capacitor. Show clearly your calculations for the two temporal regimes:  $0 < t < 3\text{msec}$  and  $3\text{msec} < t < 5\text{msec}$

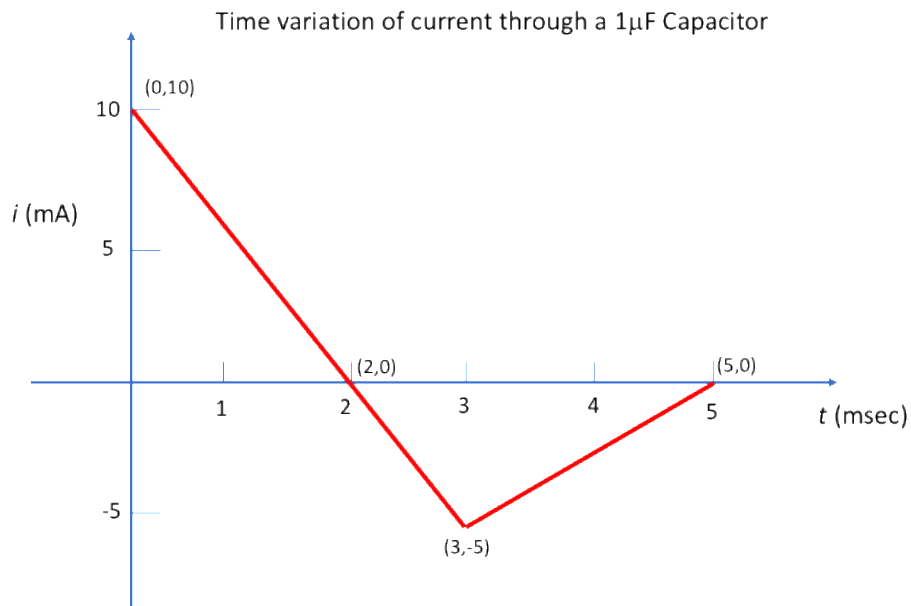


Figure 2: Current flowing into a  $1\mu\text{F}$  capacitor. Useful coordinates are shown in parenthesis

4. A current flowing through the resistor-inductor combination shown in Fig. 3 has the functional form of  $i = 5\exp(-2t)$  A, where  $t$  is time in seconds.  $R_4 = 4\Omega$  and  $L_1 = 1\text{H}$ . Calculate the total voltage across both passive elements as a function of time between  $0 < t < 2\text{s}$ . Plot both current and total voltage for this regime.

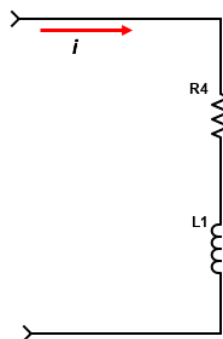


Figure 3: Resistor and Inductor in series ( $R_4 = 4\Omega$  and  $L_1 = 1\text{H}$ ) for Problem 4

5. Current flowing through the capacitor from a sinusoidal source shown in Fig. 4 has the following functional form:  $i = i_0 \cos(\omega t)$  where  $\omega$  is the angular frequency. Prove that this circuit consumes no power when averaged over an entire cycle.

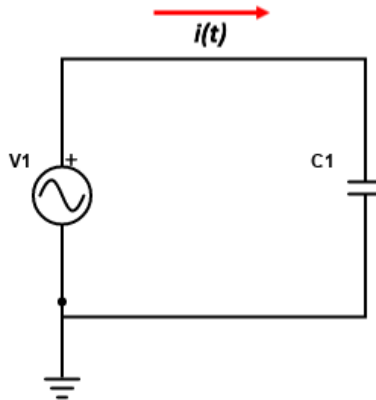


Fig 4: Voltage source V1 drives the capacitor C1 with a sinusoidal waveform

6. To work on this problem, you are encouraged to review Chapter 3 of the text (Experiments in Modern Physics by Melissinos and Napolitano), particularly Section 3.1.

Suppose you wish to detect a rapidly changing voltage signal. However, this signal is superimposed on a large DC voltage level that would damage your measuring instrument if it were in contact with it. The recommendation is to build a simple passive circuit that allows only the high-frequency signal to pass through.

- Sketch a circuit using only a resistor  $R$  and a capacitor  $C$  that would solve the problem. Indicate the points at which you can measure the input and output voltages
- Show that the magnitude of the output voltage equals the magnitude of the input voltage multiplied by

$$\frac{1}{\sqrt{1 + 1/(\omega RC)^2}}$$

where  $\omega$  is the angular frequency of the signal.

- Suppose that  $R=1\text{k}\Omega$  and the signal frequency is  $1\text{MHz}$  ( $=10^6$  cycles/s), suggest a value for the capacitor and the rationale for the choice.