

## Exam 1 Part B

● Graded

Student

Paul Lea

Total Points

52 / 80 pts

Question 1

### Method of Images

3 / 5 pts

✓ + 2 pts Recognizing a method of images problem

+ 1 pt  $\sigma = \epsilon_0 E|_{z=0}$   
or  $\sigma = -\partial V / \partial r|_{z=0}$

✓ + 1 pt  $\vec{E}(0,0,0) = -\frac{2q}{4\pi\epsilon_0 d^2} \hat{k}$

+ 1 pt  $\sigma = -6.37 \times 10^{-7} \text{ C/m}^2$

Question 2

### Gauss' Law

5 / 10 pts

✓ + 2 pts Gauss' law or Coulomb's law

+ 2 pts  $r < R: E(4\pi r^2) = \frac{1}{\epsilon_0} \frac{4}{3}\pi r^3 \rho$

+ 2 pts  $\vec{E} = \frac{\rho r}{3\epsilon_0} \hat{r}$

✓ + 2 pts  $r > R: E(4\pi r^2) = \frac{1}{\epsilon_0} \frac{4}{3}\pi R^3 \rho$

✓ + 2 pts  $\vec{E} = \frac{\rho R^3}{3\epsilon_0 r^2} \hat{r}$

💬 - 1 pt Point adjustment

1 direction?

Question 3

### Potential from field

2 / 8 pts

✓ + 2 pts  $V(r) = -\int \vec{E} \cdot d\vec{l}$

+ 2 pts  $-\int_{\infty}^R \frac{\rho R^3}{3\epsilon_0 r^2} dr$

+ 2 pts  $-\int_R^0 \frac{\rho r}{3\epsilon_0} dr$

+ 2 pts  $V(0) = \frac{\rho R^2}{2\epsilon_0}$

+ 0 pts No answer

2 The field and thus the potential is different inside and outside the sphere.

## Question 4

## Series circuit potential difference

4 / 8 pts

✓ + 2 pts Switch is open so circuit is in series and all devices have the same current

✓ + 2 pts Ohm's law:  $I = (40.0V)/(175\Omega) = 0.229A$ + 2 pts Loop rule:  $V_b - V_a = \text{emf} - V_{75\Omega}$ + 2 pts  $V_b - V_a = -2.14V$ 

+ 0 pts No answer

## Question 5

## P=VI

4 / 4 pts

✓ + 2 pts Correct power formula

✓ + 2 pts  $P = 5.73W$ 

+ 0 pts No answer

## Question 6

## Parallel circuit current

7 / 7 pts

✓ + 1 pt Switch is closed so we now have two circuits in parallel

✓ + 2 pts Ohm's law in left loop:  
 $I_{left} = (25V)/(100\Omega) = 0.250A$ ✓ + 2 pts Ohm's law in right loop:  $I_{right} = (15V)/(75\Omega) = 0.200A$ ✓ + 2 pts Kirchhoff junction rule:  
 $I_{am} = I_{left} - I_{right} = 0.050A$ 

+ 0 pts No answer

3 Please explain what you're doing or I will not give you the points next time

## Question 7

## Equivalent capacitance

6 / 6 pts

✓ + 2 pts middle branch: 3 capacitors in series so  $\frac{1}{C_{middle}} = \sum \frac{1}{C_i}$ ✓ + 1 pt  $C_{middle} = 5.29 nF$ ✓ + 2 pts Full circuit: 3 capacitors in parallel so  $C_{eq} = \sum C_i$ ✓ + 1 pt  $C_{eq} = 19.3 nF$ 

+ 0 pts No answer

## Question 8

## Total system charge

5 / 5 pts

✓ + 2 pts  $Q = C\Delta V$ ✓ + 2 pts  $Q_{tot} = C_{eq}V$ ✓ + 1 pt  $Q_{tot} = 482 \text{ nC}$ + 0 pts [Click here to replace this description.](#)

## Question 9

## Capacitor charge

6 / 6 pts

✓ + 2 pts Capacitors are in parallel so they are at the same potential

✓ + 2 pts  $Q_{6.5} = C_{6.5}V$ ✓ + 2 pts  $Q_{6.5} = 162 \text{ nC}$ + 0 pts [Click here to replace this description.](#)

## Question 10

## Potential difference across capacitor in series

2 / 6 pts

+ 2 pts Capacitors in series have the same charge

✓ + 2 pts  $Q = C_{eq}V = (5.29 \text{ nF})(25V) = 132.25 \text{ nC}$ + 2 pts  $V_{10} = \frac{Q}{C_{10}} = 13.2V$ + 0 pts [Click here to replace this description.](#)

## Question 11

## Field from potential

5 / 5 pts

✓ + 2 pts  $\vec{E} = -\vec{\nabla}V$ ✓ + 3 pts  $\vec{E} = -z\hat{i} - 2y\hat{j} - x\hat{k}$ 

+ 0 pts No answer

## Question 12

## Gauss' law in differential form

3 / 5 pts

✓ + 3 pts  $\vec{\nabla} \cdot \vec{E} = \frac{\rho}{\epsilon_0}$ + 2 pts  $\vec{\nabla} \cdot \vec{E} = -2\epsilon_0$ 

+ 0 pts No answer

Question 13

Work

0 / 5 pts

+ 2 pts  $W = Q\Delta V$

+ 1 pt  $\Delta V = V(1, 2, 3) - V(\infty) = V(1, 2, 3)$   
( $V(\infty) = 0$ )


+ 2 pts  $W = 7Q$

✓ + 0 pts Click here to replace this description.

Name: Paul Le-

Part II: Problems - Include a logical statement or relevant equation for full credit

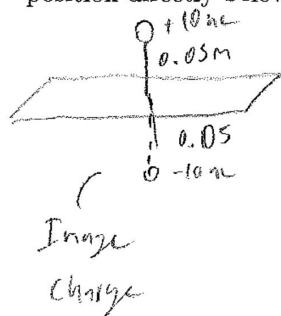**Problem 1.** A charge of  $+10.0 \text{ nC}$  is placed a distance of  $0.050 \text{ meters}$  above a very large, flat, grounded, conducting sheet. Calculate the surface charge density on the sheet at a position directly below the charge.



$$\begin{aligned}\vec{E}_t &= \vec{E}_+ + \vec{E}_- \\ &= \frac{20 \times 10^{-9}}{4\pi\epsilon_0 (0.05)^2} \hat{k} \\ &= 7.19 \times 10^3 \text{ N/C} \hat{k}\end{aligned}$$

**Problem 2.** A solid ball of charge with uniform volume charge density  $\rho$  and radius  $R$  is centered at the origin.

a) Calculate the electric field inside and outside the ball.

$E_{\text{inside}} = 0$   
b/c no flux  
through  
surface  
inside  
sphere

Outside:  $R < r$

$$q_{\text{enc}} = \rho \frac{4}{3} \pi R^3$$

$$\vec{E} = \frac{1}{4\pi\epsilon_0} \frac{\rho \frac{4}{3} \pi R^3}{r^2}$$

$$\vec{E} = \frac{\rho \frac{4}{3} \pi R^3}{12\pi\epsilon_0 r^2}$$

$r$  - distance from center of ball / origin


b) Calculate the electric potential at the origin using a reference at infinity.

$$V = k \frac{q}{r} = k \frac{\rho \frac{4}{3} \pi R^3}{r}$$

Name: Paul Lee

**Problem 3.** The figure displays an electrical circuit. All components are ideal.

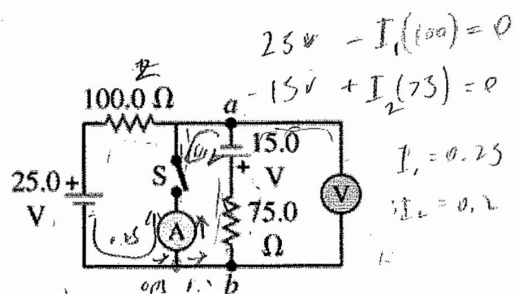a) Find the potential difference measured by the voltmeter with the switch open as shown.



$$\sum_{i=1}^N \Delta V_i = 0$$

$$\sum_{i=1}^N I_i = 0$$

$$25 - 75 I_1 + 15 + 100 I_2 = 0$$

$$V_{ab} = 75(0.2) - 15 = 0$$

$$V_{ab} = 0$$

b) Find the power supplied by the 25 V battery to the circuit when the switch is open.

$$P = I V$$

$$P = 0.25(25)$$

$$P = 6.25 \text{ W}$$

c) Find the current measured by the ammeter with the switch closed.

$$0.25 - 0.2 = 0.05 \text{ A}$$

Name: Paul Lea

**Problem 4.** For the system of capacitors shown in the figure, a potential difference of 25 V is maintained across  $ab$

a) What is the equivalent capacitance of this system between  $a$  and  $b$ ?


Series  $\frac{1}{C_t} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$

$$\frac{1}{C_t} = \frac{1}{18} + \frac{1}{30} + \frac{1}{10} = \frac{17}{90} = \frac{1}{C_t} \rightarrow C_t = \frac{90}{17} = 5.29 \text{ nF}$$

Parallel

$$C_t = C_1 + C_2 + \dots$$
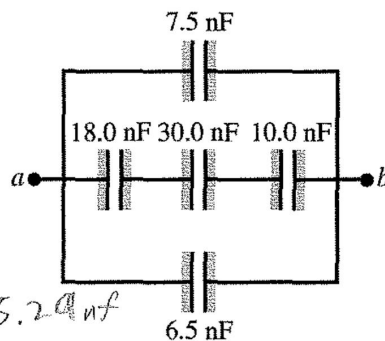
$$C_t = 5.29 + 7.5 + 6.5 = 19.29 \text{ nF}$$



b) How much charge is stored by this system?

$$Q = C \Delta V$$

$$19.29(25) = 482.25$$

$$Q = 482.25 \text{ nC}$$

c) How much charge does the 6.5 nF capacitor store?

$$Q = C \Delta V$$

$$6.5(25)$$

$$Q = 162.5 \text{ nC}$$

d) What is the potential difference across the 10 nF capacitor?

$$V_t = V_1 + V_2 + \dots$$

$$Q_t = 5.29 \cdot 25 \text{ V}$$

$$\frac{132.25 \text{ nC}}{5.29 \text{ nF}} = \frac{Q}{18} + \frac{Q}{30} + \frac{Q}{10}$$

$$Q = 102.25$$

$$V_3 = \frac{44.045 \text{ nC}}{10 \text{ nF}} = 4.408 \text{ V}$$

Name: Paul Le

**Problem 5.** The electric potential with respect to infinity inside a sphere with radius  $R = 10$  m is given by the function  $V(x, y, z) = xz + y^2$

a) What is the electric field inside the sphere?

$$\vec{E} = -\nabla V$$
$$\vec{E} = -\langle z, 2y, x \rangle$$

b) What is the volume charge density inside the sphere?

$$\vec{\nabla} \cdot \vec{E} = \frac{\rho}{\epsilon_0}$$
$$\epsilon_0 (\vec{\nabla} \cdot \vec{E}) = \rho$$
$$z^2 + (2y)^2 + 1^2$$
$$z^2 + 4y^2 + 1^2 = C$$

c) How much work would be required to bring a point charge  $+Q$  from  $\infty$  to  $(1, 2, 3)$ ?